

An introduction to Junction Field Effect Transistors (JFETs)

The Junction Field Effect Transistor (JFET) exhibits characteristics which often make it more suited to a particular application than the bipolar transistor. Some of these applications are:

- Displacement sensors
- High input impedance amplifiers
- Low-noise amplifiers
- Differential amplifiers
- Constant current sources
- Analogue switches or gates
- Voltage controlled resistors



Basic JFET amplifier configurations

There are three basic JFET circuits: the common source, the common gate, and the common drain as shown in figure 1. Each circuit configuration describes a two port network having an input and an output. The transfer function of each is also determined by the input and output voltages or currents of the circuit.

The most common configuration for the JFET as an amplifier is the common source circuit. For an N-channel device the circuit would be biased as shown in figure 2.

Figure 1 – Basic JFET amplifier circuit configurations


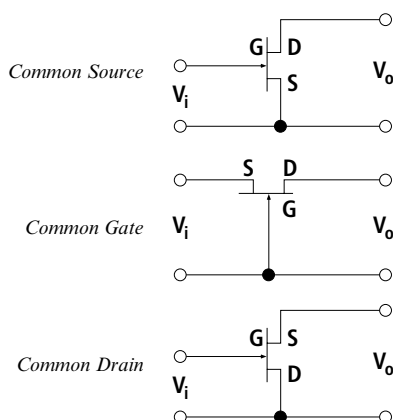


Figure 2 – Basic common source amplifier circuit biasing configuration

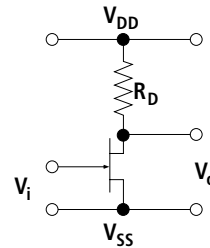


Circuit biasing configuration

Since the N-channel JFET is a depletion mode device and is normally on, a gate voltage which has a negative polarity with respect to the source is required to modulate or control the drain current. This negative voltage can be provided by a single positive power supply using the self biasing method shown in figure 3. This is accomplished by the voltage which is dropped across the source resistor, R_s , according to the current flowing through it. The gate-to-source voltage is then defined as:

$$(1) V_{GS} = I_D \times R_S$$

The circuit of figure 3 also defines a basic single stage JFET amplifier. The source resistor value is determined by selecting the bias point for the circuit from the characteristic curves of the JFET being used. The value of the drain resistor is then chosen from the required gain of the amplifier and the value of the drain current which was previously selected in determining the gate voltage. The value of this resistor must also allow the circuit to have sufficient dynamic range, or voltage swing, required by the following stage.

Figure 3 – Common source amplifier using VGS self-biasing method

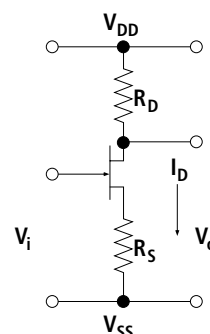

An introduction to Junction Field Effect Transistors (JFETs) cont.

The following stage could be anything from another identical circuit to a loud speaker for an audio system. The voltage gain of this circuit is then defined as:

$$(2) A_V = (g_m \times Z_L) / (1 + g_m \times R_S)$$

where A_V = the voltage gain
 g_m = the forward transconductance or gain of the JFET
 Z_L = the equivalent load impedance
 R_S = the value of the source resistor

The effect of the source resistor on the gain of the circuit can be removed at higher frequencies by connecting a capacitor across the source resistor. This then results in an amplifier which has a gain of:

$$(3) A_V = g_m \times Z_L$$

but only at frequencies above that defined by the resistor-capacitor network in the source circuit.

This frequency is defined as:

$$(4) f_{lo} = 1 / (2\pi \times R_S \times C_S)$$

where f_{lo} = the low frequency corner
 π = the constant 3.1418
 R_S = the value of the source resistor in ohms
 C_S = the value of the source capacitor in farads


This circuit also has a high input impedance, generally equal to the value of the input impedance of the JFET.

A low-noise amplifier

A minor change to the circuit of figure 3 describes a basic single stage low-noise JFET amplifier. Figure 4 shows that this change only incorporates a resistor from the gate to Vss. This resistor supplies a path for the gate leakage current in an AC coupled circuit. Its value is chosen by the required input impedance of the amplifier and its desired low-noise characteristics.


The noise components of this amplifier are the thermal noise of the drain and gate resistors plus the noise components of the JFET. The noise contribution of the JFET is from the shot noise of the gate leakage current, the thermal noise of the channel resistance, and the frequency noise of the channel.

Figure 4 – Low noise JFET single stage amplifier with source by-pass capacitor, CS

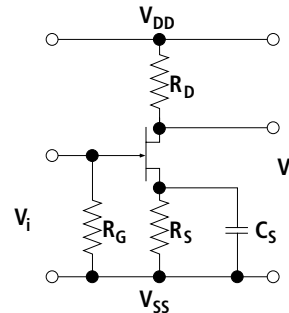

These noise characteristics are generally lower than those found in bipolar transistors if the JFET is properly selected for the application. The voltage gain of the circuit is again defined by equation (3).

Figure 5 – The matched pair JFET differential amplifier

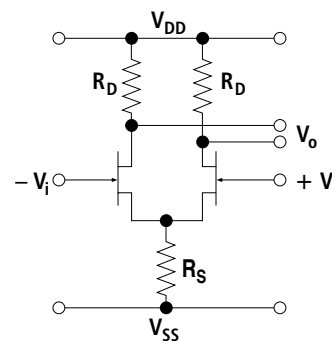


The JFET differential amplifier

Another application of the JFET is the differential amplifier. This configuration is shown in figure 5. The differential amplifier requires that the two transistors be closely matched electrically and physically located near each other for thermal stability. Either input and either output can be used or both inputs and only one output and conversely only one input and both outputs can be used.

An introduction to Junction Field Effect Transistors (JFETs) cont.

Figure 6 – JFET constant current source

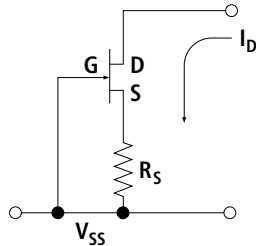

For the configuration shown the source resistor is chosen to determine the gate to source bias voltage, remembering that the current will be twice that of each of the JFET drain currents. The value of the drain resistors is chosen to provide a suitable dynamic range at the output. The gain of this circuit is defined by:

$$(5) A_v = 2x (g_m \times R_i) / (1 + g_m \times R_s)$$

where the terms in the equation have already been defined.

This circuit configuration is very useful as a high input impedance stage to be connected to the input of a low cost operational amplifier, such as the popular 741 Op-Amp.

The JFET constant current source

A constant current source using a JFET is shown in figure 6. This circuit configuration has many useful applications ranging from charging circuits for integrators or timers to replacing the source resistor in the differential amplifier shown in figure 5. The current provided by the constant current source of figure 6 is defined as:

$$(6) I_D = I_{DSS} [1 - (V_{GS} / V_p)]^2$$

where I_D = the drain current or magnitude of current sourced

I_{DSS} = the drain saturation current of the JFET

V_{GS} = $I_D \times R_S$

V_p = the JFET pinch-off voltage

2 = the squared value of the term in brackets

It can be readily seen that the use of this circuit in the source circuit of the differential amplifier of figure 5 would improve the circuit voltage gain as well as reduce the amplifier noise and enhance the CMRR of the amplifier.

The JFET analogue switch

Figures 7, 8, and 9 show three different applications for the JFET to be used as an analogue switch or gate. Figures 7 and 8 both demonstrate methods for realising programmable gain amplifiers, while figure 9 shows an analogue multiplexer circuit using JFETs and a common op-amp integrated circuit.

It can be seen from figure 7 that the gain of the stage can be changed by switching in any combination of feedback resistors R1 through Rn. The JFET in series with the input resistor should be of the same type as those in the feedback paths and is used for thermal stability of the circuit gain. The transfer function of the circuit of figure 7 is approximated by:

$$(7) V_o / V_i = 1 / [(1 / R_1) + (1 / R_2) + \dots + (1 / R_n)] / R_i$$

where R_1 through R_n = the feedback resistors


R_i = the input resistors

V_o = the output voltage

V_i = the input voltage

Note that only those feedback resistors which are switched into the circuit are to be included in the the transfer function equation.

Figure 7 – Programmable gain amplifier

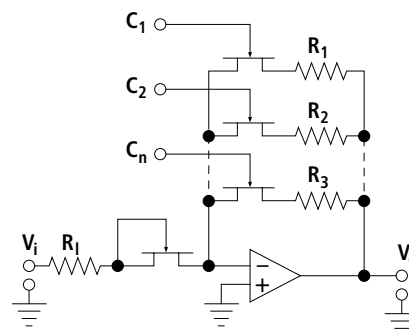

The circuit of figure 8 shows another method to realise a programmable gain amplifier using a common op-amp, four resistors, and only two JFETs. The gain of this circuit can also be changed by switching in the desired resistors by turning off the appropriate JFET thus switching in the parallel resistor. The transfer function of this circuit is approximated by:

$$(8) V_o / V_i = (R_3 + R_4) / (R_1 + R_2)$$

An introduction to Junction Field Effect Transistors (JFETs) cont.

Figure 8 – Programmable gain amplifier with four resistors and two JFETs


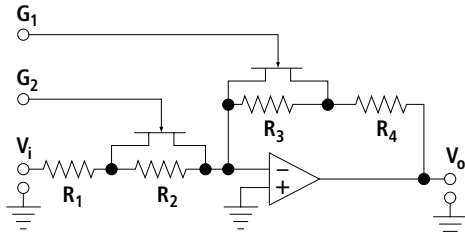


Figure 9 – Analogue multiplexer circuit which can also be used as a programmable summing amplifier

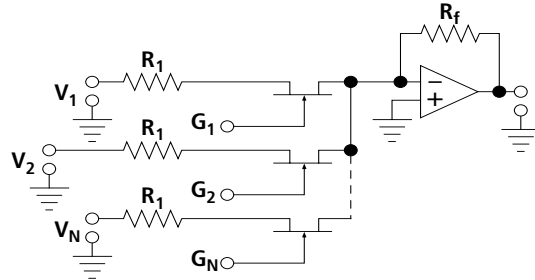

It should be noted that only those resistors which are switched into the circuit are to be included in the transfer function equation.

Figure 9 shows a circuit in which the JFETs are acting as analogue switches to multiplex several input signal sources to a single output source. The transfer function of this circuit is then approximated by:

$$(9) \ V_o / V_i = R_f / R_n$$

where R_f = the feedback resistor
 R_n = any one of the input resistors

Further examination of this circuit shows that it can also be used as a programmable summing amplifier by switching in any combination of input signals. The transfer function is then approximated by:

$$(10) \ V_o / V_i = (R_f / R_1) + (R_f / R_2) + \dots + (R_f / R_n)$$

Again in this application only those resistors which are switched into the circuit are to be included in the transfer function equation.

